

Embedded Systems 1

Lab Report 1

Gavin McKim

2/28/2019

Purpose:

The purpose of this lab is to get used to utilizing and implementing vhdl code. The lab introduces the basics of writing source code and testing it with testbench code. It does this while also introducing the basic building blocks of many digital circuits. Specifically, the lab introduces the counter and walks us through the many uses of it. It walks us through the many creative ways to use a counter to solve problems.

1. My Clock is Just Right

Theory

In this first part, the circuit should be able to take an input signal with a frequency of 125MHz, and step it down into a signal with a frequency of 2Hz. It does this using a counter. The counter increments up on every rising edge of the 125MHz clock. When the counter reaches 62.5M, the circuit outputs a pulse and resets the counter. 62.5M is used since it is the ratio between 125 MHz and 2 Hz. This design should output a pulse at a frequency of 2 Hz. In other words, it should output a pulse every 0.5 seconds.

Design

Code:

divider_top.vhd *

/home/user/Desktop/project_1/project_1.srscs/sources_1/imports/sources_1/imports/project_1.srscs/sources_1/new/divider_top.vhd



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5
6  entity clock_div is
7  port (
8      clk_in : in std_logic;
9      div : out std_logic
10 );
11 end clock_div;
12
13 architecture cnt of clock_div is
14     signal count : std_logic_vector (25 downto 0) := (others => '0');
15     begin
16     process(clk_in) begin
17         if rising_edge(clk_in) then
18             count <= std_logic_vector( unsigned(count) + 1);
19
20             if ( count="11101110011010110010100000") then
21                 div <= '1';
22                 count <= (others => '0');
23
24             else
25                 div <= '0';
26             end if;
27
28         end if;
29     end process;
30
31     end cnt;
32
33     library ieee;
34     use ieee.std_logic_1164.all;
35     use ieee.numeric_std.all;
36
37     entity divider_top is
38     Port ( clk : in std_logic;
39           Q : out std_logic);
40     end divider_top;
41
42     architecture Behavioral of divider_top is
43
44     component clock_div is
45     port (
46         clk_in : in std_logic;
47         div : out std_logic
48     );
49     end component;
50
51     signal D, CE : std_logic := '0';
52
53     begin
54
55     di: clock_div
56     port map ( clk_in => clk,
57               div => CE);
58
59     reg: process(clk)
60     begin
61         if (rising_edge(clk)) then
62             if(CE = '1') then
63                 D <= not D;
64             end if;
65         end if;
66     end process;
67     Q <= D;
68
69     end Behavioral;
70
```


Test

Test Bench

/home/user/Desktop/project_1/project_1.srds/sim_1/imports/sim_1/imports/new/testbench.vhd

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity counter_tb is
5  end counter_tb;
6
7  architecture tb of counter_tb is
8
9      component counter
10     port (
11         clk : in std_logic;
12         newf : out std_logic
13         --cnto : out std_logic_vector (25 downto 0)
14     );
15 end component;
16
17 signal tb_clk : std_logic := '0';
18 signal tb_cnt : std_logic := '0';
19 --signal test : std_logic_vector (25 downto 0) := (others => '0');
20
21 begin
22
23     dut: counter port map (clk => tb_clk, newf => tb_cnt);
24
25     process begin
26         tb_clk <= '0';
27         wait for 4 ns;
28         tb_clk <= '1';
29         wait for 4 ns;
30     end process;
31
32 end tb;
```


Simulation

 


As you can see, the circuit outputs a pulse every 500 ms or 0.5 seconds.

Implementation

RTL Schematic

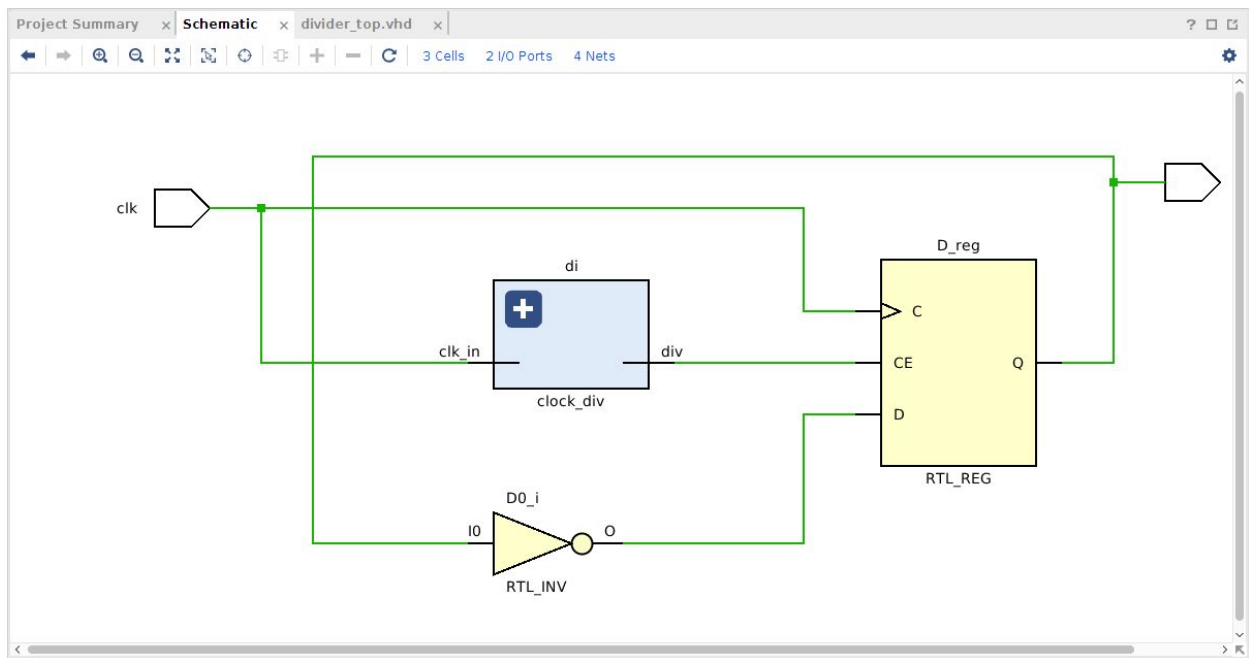


Synthesis Schematic

 

Post-Synthesis Utilization Table

Utilization		Post-Synthesis Post-Implementation			
		Graph Table			
Resource	Estimation	Available	Utilization %		
LUT	10	17600	0.06		
FF	28	35200	0.08		
IO	2	100	2.00		
BUFG	1	32	3.13		

On-Chip Power Graph

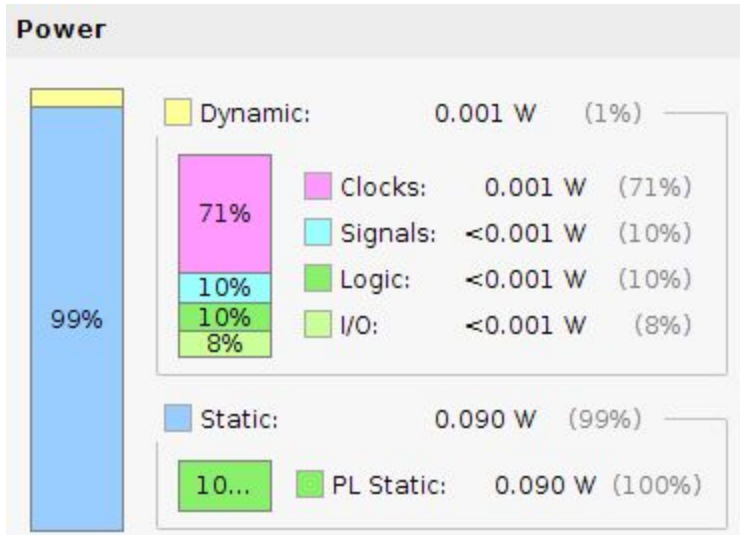

Constraint File

/home/user/Desktop/project_1/project_1.srscs/constrs_1/new/top_constraint.xdc

```

1  ##Clock signal
2  set_property -dict { PACKAGE_PIN L16  IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L11P_T1_SRCC_35 Sch=sysclk
3  create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports { clk }];
4
5
6  ##Switches
7  set_property -dict { PACKAGE_PIN G15  IOSTANDARD LVCMOS33 } [get_ports { swt[0] }]; #IO_L19N_T3_VREF_35 Sch=SW0
8  set_property -dict { PACKAGE_PIN P15  IOSTANDARD LVCMOS33 } [get_ports { swt[1] }]; #IO_L24P_T3_34 Sch=SW1
9  set_property -dict { PACKAGE_PIN W13  IOSTANDARD LVCMOS33 } [get_ports { swt[2] }]; #IO_L4N_T0_34 Sch=SW2
10 set_property -dict { PACKAGE_PIN T16  IOSTANDARD LVCMOS33 } [get_ports { swt[3] }]; #IO_L9P_T1_DQS_34 Sch=SW3
11
12
13 ##Buttons
14 set_property -dict { PACKAGE_PIN R18  IOSTANDARD LVCMOS33 } [get_ports { button[0] }]; #IO_L20N_T3_34 Sch=BTN0
15 set_property -dict { PACKAGE_PIN P16  IOSTANDARD LVCMOS33 } [get_ports { button[1] }]; #IO_L24N_T3_34 Sch=BTN1
16 set_property -dict { PACKAGE_PIN V16  IOSTANDARD LVCMOS33 } [get_ports { button[2] }]; #IO_L18P_T2_34 Sch=BTN2
17 set_property -dict { PACKAGE_PIN Y16  IOSTANDARD LVCMOS33 } [get_ports { button[3] }]; #IO_L7P_T1_34 Sch=BTN3
18
19
20 ##LEDs
21 set_property -dict { PACKAGE_PIN M14  IOSTANDARD LVCMOS33 } [get_ports { Q }]; #IO_L23P_T3_35 Sch=LED0
22 set_property -dict { PACKAGE_PIN M15  IOSTANDARD LVCMOS33 } [get_ports { led[1] }]; #IO_L23N_T3_35 Sch=LED1
23 set_property -dict { PACKAGE_PIN G14  IOSTANDARD LVCMOS33 } [get_ports { led[2] }]; #IO_0_35=Sch=LED2
24 set_property -dict { PACKAGE_PIN D18  IOSTANDARD LVCMOS33 } [get_ports { led[3] }]; #IO_L3N_T0_DQS_AD1N_35 Sch=LED3

```

2. Bouncy Buttons

Theory

The second part of the lab presents another usage for the flexible counter. Buttons are mechanical devices that use a spring to pop back up after they are pushed. However, they do not perfectly rise back up. After being pushed, the spring jumps back up and oscillates before returning to its steady state. This presents a problem in digital circuit design. In digital circuits,

this oscillation creates unwanted inputs as the springs bounces across the border of a logic high and a logic low. To fix this problem, the lab presents a debouncer circuit using a counter. This circuit works by incrementing a counter while the button input remains a logic '1'. If an input comes in a logic '0', the counter is reset. When the counter reaches a certain value, it stop incrementing and outputs a '1'.

Design

Code:

/home/user/Desktop/project_1/project_1.srscs/sources_1/imports/sources_1/imports/project_1.srscs/sources_1/new/debouncer.vhd

```
1
2 library ieee;
3 use ieee.std_logic_1164.all;
4 use ieee.numeric_std.all;
5
6
7 entity debouncer is
8   Port ( clk, btn : in std_logic;
9         debounce: out std_logic);
10 end debouncer;
11
12 architecture Behavioral of debouncer is
13
14   signal count : std_logic_vector (21 downto 0) := (others => '0');
15   signal samp : std_logic_vector (1 downto 0) := (others => '0');
16
17   begin
18   process(clk) begin
19     if rising_edge(clk) then
20
21       samp(1) <= samp(0);
22       samp(0) <= btn;
23
24       if(samp(1) = '1') then
25         if(count /= "1001100010010110100000") then
26           count <= std_logic_vector( unsigned(count) + 1);
27         end if;
28
29         if(count = "1001100010010110100000") then
30           debounce <= '1';
31         end if;
32       else
33         count <= (others => '0');
34         debounce <= '0';
35       end if;
36
37     end if;
38   end process;
39 end Behavioral;
40
41
42
```

Test


Test Bench

/home/user/Desktop/project_1/project_1.srscs/sim_1/imports/sim_1/imports/new/debounce_tb.vhd



```
1
2 library IEEE;
3 use IEEE.STD_LOGIC_1164.ALL;
4 use IEEE.NUMERIC_STD.ALL;
5
6
7 entity debounce_tb is
8
9 end debounce_tb;
10
11 architecture tb of debounce_tb is
12
13 component debouncer is
14   Port ( clk, btn : in std_logic;
15         debounce: out std_logic);
16 end component;
17
18   signal tb_clk : std_logic := '0';
19   signal tb_btn : std_logic := '0';
20   signal tb_deb : std_logic := '0';
21
22 begin
23
24   deb: debouncer port map (clk => tb_clk, btn => tb_btn, debounce => tb_deb);
25
26 process begin
27   tb_clk <= '0';
28   wait for 4 ns;
29   tb_clk <= '1';
30   wait for 4 ns;
31 end process;
32
33 process begin
34   tb_btn <= '1';
35   wait for 25 ms;
36   tb_btn <= '0';
37   wait for 10 ms;
38 end process;
39
40 end tb;
41
```

Simulation

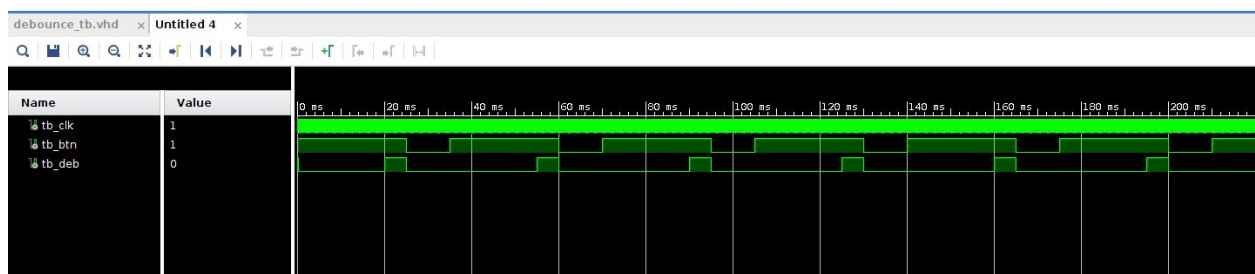

As seen in the test bench, when the button is pushed for 25ms, it is off for the first 20 ms while the counter is incrementing. When the counter reaches the desired value, the debouncer outputs a '1' for the remaining 5ms that the button is held.

3. Actually Using a Counter to Count

Theory

This part of the lab is pretty self-explanatory. We use our basic counter to design a complete 4-bit counter. The 4-bit counter has two inputs to enable functionality in the device. It also has a reset input that sets the output count to 0. The 4-bit counter can count up or down depending on the signal going into the dir input. The dir input is only updated when the updn input is '1'. You can load the value being sent into the val input into the device by sending a logic '1' to the ld input. The counter will count up to this value and then reset to 0. Or, if it is decrementing, it will count down to 0 before going back to the value.

Design

Code

/home/user/Desktop/project_1/project_1.srscs/sources_1/imports/sources_1/imports/project_1.srscs/new/project_1.srscs/sources_1/new/fancy_counter.vhd

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5
6  entity fancy_counter is
7      Port ( en, clk, clk_en : in std_logic;
8            dir, ld, rst, updn : in std_logic;
9            val : in std_logic_vector (3 downto 0);
10           cnt : out std_logic_vector (3 downto 0) := (others => '0'));
11 end fancy_counter;
12
13 architecture fc of fancy_counter is
14
15     signal count : std_logic_vector (3 downto 0) := "0000";
16     signal value : std_logic_vector (3 downto 0) := "1111";
17     signal direct : std_logic := '1';
18
19     begin
20
21     process(clk) begin
22
23     if rising_edge(clk) then
24         if(en = '1') then
25
26             if(rst = '1') then
27                 count <= (others => '0');
28             end if;
29
30             if(clk_en = '1') then
31
32                 if(rst = '1') then
33                     count <= (others => '0');
34                 end if;
35
36                 if(ld = '1') then
37                     value <= val;
38                 end if;
39
40                 if(updn = '1') then
41                     direct <= dir;
42                 end if;
43
44                 if(direct = '1') then
45                     if(count = value) then
46                         count <= (others => '0');
47                     else
48                         count <= std_logic_vector( unsigned(count) + 1);
49                     end if;
50
51                 else
52                     if(count = "0000") then
53                         count <= value;
54                     else
55                         count <= std_logic_vector( unsigned(count) - 1);
56                     end if;
57                 end if;
58
59             end if;
60         end if;
61     end if;
62 end if;
63
64     cnt <= count;
65 end process;
66 end fc;
67
```

4. Bringing It All Together

Theory

This part of the lab brings together all the parts designed in the previous sections of the lab. The final put together circuit is designed to be able to be implemented on a Zybo Board. The buttons on the board are fed into our debouncers to provide an accurate input signal. The output of these buttons are fed into the 4-bit counter. Switches on the board are used to control the val input on the 4-bit counter board and the clock divider is used to send a 2 Hz signal to one of the enabler inputs. Finally, the count output of the 4-bit counter is displayed using leds.

Design

Code

```

164
165 library IEEE;
166 use IEEE.STD_LOGIC_1164.ALL;
167 use IEEE.NUMERIC_STD.ALL;
168
169 entity top_design is
170     Port ( button, swt : in std_logic_vector(3 downto 0);
171           clk : in std_logic;
172           led : out std_logic_vector(3 downto 0));
173 end top_design;
174
175 architecture td of top_design is
176
177     component clock_div is
178     port (
179         clk_in : in std_logic;
180         div : out std_logic
181     );
182 end component;
183
184     component debouncer is
185     Port ( clkd, btn : in std_logic;
186           debounce: out std_logic);
187 end component;
188
189     component fancy_counter is
190     Port ( en, clkf, clk_en : in std_logic;
191           dir, ld, rst, updn : in std_logic;
192           val : in std_logic_vector (3 downto 0);
193           cnt : out std_logic_vector (3 downto 0));
194 end component;
195
196     signal dbnc : std_logic_vector (3 downto 0);
197     signal temp_div : std_logic;
198
199     begin
200
201
202     u1: debouncer
203     port map ( btn => button(0),
204               clkd => clk,
205               debounce => dbnc(0));
206
207     u2: debouncer
208     port map ( btn => button(1),
209               clkd => clk,
210               debounce => dbnc(1));
211
212     u3: debouncer
213     port map ( btn => button(2),
214               clkd => clk,
215               debounce => dbnc(2));
216
217     u4: debouncer
218     port map ( btn => button(3),
219               clkd => clk,
220               debounce => dbnc(3));
221
222     u5: clock_div
223     port map ( clk_in => clk,
224               div => temp_div);

```


```

224
225 u6: fancy_counter
226 port map ( clkf => clk,
227            clk_en => temp_div,
228            rst => dbnc(0),
229            en => dbnc(1),
230            updn => dbnc(2),
231            ld => dbnc(3),
232            dir => swt(0),
233            val => swt,
234            cnt => led);
235
236 end td;
237


```

Implementation

RTL Design

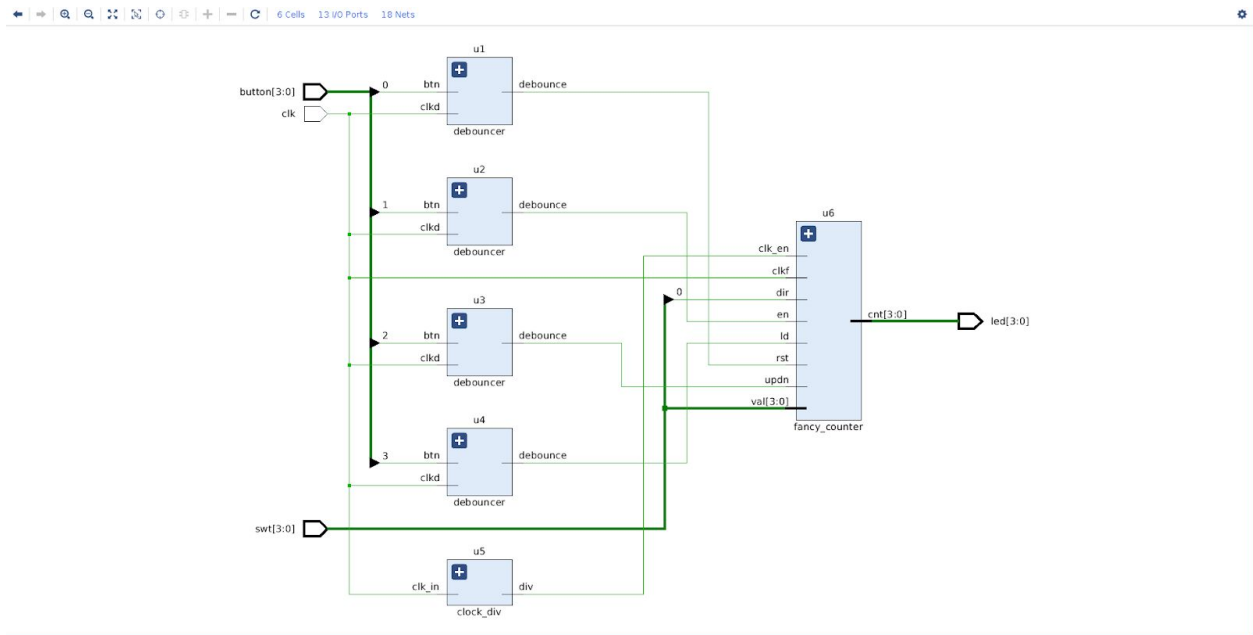


Synthesis Schematic

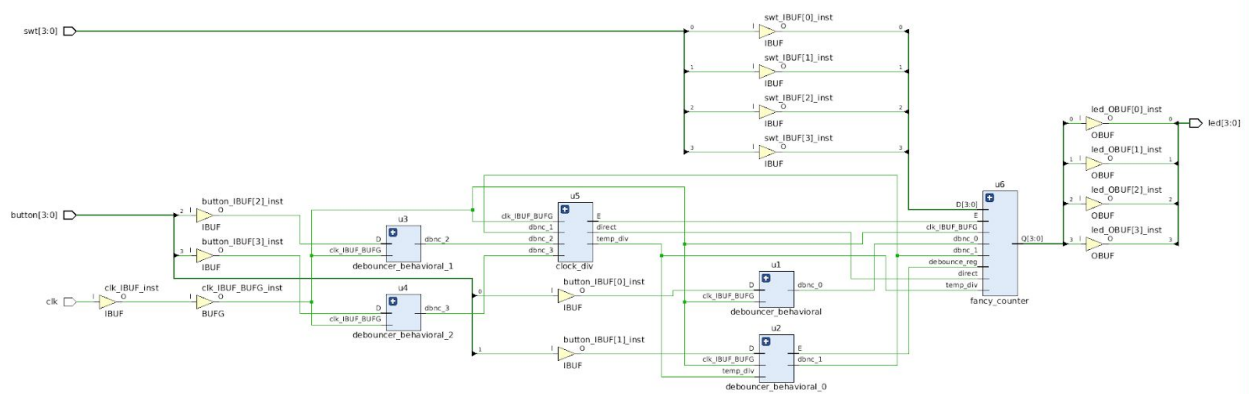

Post-Synthesis Utilization Table

Utilization		Post-Synthesis Post-Implementation		
		Graph Table		
Resource	Estimation	Available	Utilization %	
LUT	62	17600	0.35	
FF	136	35200	0.39	
IO	13	100	13.00	
BUFG	1	32	3.13	

On-Chip Power

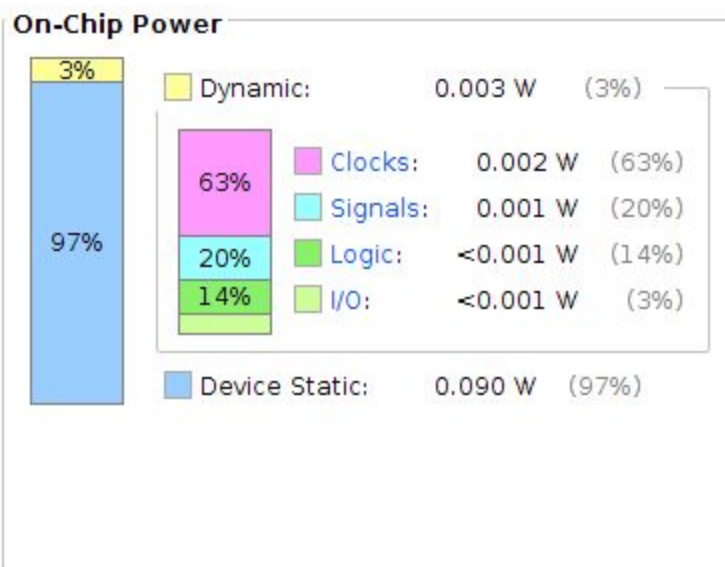

Constraint File

/home/user/Desktop/project_1/project_1.srscs/constrs_1/new/top_constraint.xdc

```
1  ##Clock signal
2  set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L11P_T1_SRCC_35 Sch=sysclk
3  create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports { clk }];
4
5
6  ##Switches
7  set_property -dict { PACKAGE_PIN G15 IOSTANDARD LVCMOS33 } [get_ports { swt[0] }]; #IO_L19N_T3_VREF_35 Sch=SW0
8  set_property -dict { PACKAGE_PIN P15 IOSTANDARD LVCMOS33 } [get_ports { swt[1] }]; #IO_L24P_T3_34 Sch=SW1
9  set_property -dict { PACKAGE_PIN W13 IOSTANDARD LVCMOS33 } [get_ports { swt[2] }]; #IO_L4N_T0_34 Sch=SW2
10 set_property -dict { PACKAGE_PIN T16 IOSTANDARD LVCMOS33 } [get_ports { swt[3] }]; #IO_L9P_T1_DQS_34 Sch=SW3
11
12
13 ##Buttons
14 set_property -dict { PACKAGE_PIN R18 IOSTANDARD LVCMOS33 } [get_ports { button[0] }]; #IO_L20N_T3_34 Sch=BTN0
15 set_property -dict { PACKAGE_PIN P16 IOSTANDARD LVCMOS33 } [get_ports { button[1] }]; #IO_L24N_T3_34 Sch=BTN1
16 set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports { button[2] }]; #IO_L18P_T2_34 Sch=BTN2
17 set_property -dict { PACKAGE_PIN Y16 IOSTANDARD LVCMOS33 } [get_ports { button[3] }]; #IO_L7P_T1_34 Sch=BTN3
18
19
20 ##LEDs
21 set_property -dict { PACKAGE_PIN M14 IOSTANDARD LVCMOS33 } [get_ports { led[0] }]; #IO_L23P_T3_35 Sch=LED0
22 set_property -dict { PACKAGE_PIN M15 IOSTANDARD LVCMOS33 } [get_ports { led[1] }]; #IO_L23N_T3_35 Sch=LED1
23 set_property -dict { PACKAGE_PIN G14 IOSTANDARD LVCMOS33 } [get_ports { led[2] }]; #IO_0_35=Sch=LED2
24 set_property -dict { PACKAGE_PIN D18 IOSTANDARD LVCMOS33 } [get_ports { led[3] }]; #IO_L3N_T0_DQS_ADIN_35 Sch=LED3
```

Discussion

Questions

1.1. How much do we need to divide our input by to get from 125 MHz to 2 Hz?

$$125/x = 2 \rightarrow x = 62.5\text{MHz}$$

1.2 How many bits are required to store a counter that can count up to the value obtained in Q1.1?

When converting 62.5MHz you get a binary number that takes 26 bits.

Question 2.1: What is the value of the button when it is pressed for the Zybo?

When a button is pressed the Zybo inputs a logic '1'

Question 2.3: If we want our debounce time to be 20 ms, and our system clock is 125 MHz, how many ticks do we need a steady '1' to be read for it to count as a '1' ?

125 MHz is in ticks/second. So in order to get the number of ticks we multiply 125 MHz with 20 ms. This gives us 2500000 ticks.

Question 2.4: How many bits are required for a counter that can go that high?

The counter needs 22 bits.

Observations

Although a little confusing at times, the lab did a pretty good job of introducing me to designing digital circuits. Through trial and error I have learned about many mistakes that one could make when coding in VHDL and how to avoid them. I've also gotten more comfortable with using port mapping in VHDL. Before this lab I thought I had to copy my entire component code into the overall design file. Near the end I realized that you can map to other source files without having to migrate the whole code. Additionally, the lab helped me get accustomed with counters and how to use them. I now have a glimpse into how counters can be used and will keep them in mind when designing new digital circuits.

Questions

After finishing the lab, I feel that I have a pretty good understanding of how VHDL works and is implemented. One thing I still do not completely understand is errors in code. Often times, I have a hard time understanding where the error is coming from and when the issue is. For example, when simulating my fancy_counter, my count signal was displaying a value of X. This means that it was getting conflicting values sent to it. I managed to fix it but I am unsure what I did. I believe it has something to do with my multiple processes inside my test bench but I am unsure of the exact issue. Following up on that, I am a little unsure about how test benches and multiple simultaneous processes work.